

ASPICE notes

drx

H-1

Aspice manual

table of contents

p2-2(52) quickAC.sp

8-2(312) .OPTIONS LIST NODE POST

9-6(360) .OP

11-4(456) .AC dec 10 1k 1Meg

7-4(250) ~~at~~ .print ac v(1) v(2) i(r2) i(c1)

5-6(152) v1 1 0 10 ac 1

4-2(120) r1 1 2 1k

r2 2 0 1k

4-4(122) c1 2 0 .001u

.end

hspice quickAC.sp > quickAC.lis


quickAC.acf binary for GVI output

.icf initial conditions

.stop status

.lis output

2-7(57) quickINV.sp

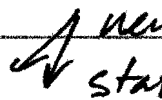10-4(412) .tran 200p 20N  new statements

17-4(730) m1 out in VCC VCC pch L=1u W=20u
VCC VCC 0 5

5-7(153) Vin in 0 0 PULSE .2 4.8 2N 1N 1N 5N 20N

3-29(87) .model pch pmos |level|=1

18-1[†](845)

dra

H-2

InvChain.sp

new statements

3-32 (90)

.lib 'cmoslibrary.lib' nominal

3-19 (77)

.global vcc! gnd!

3-11~~3~~ (41)

.subckt inv A z

m1 z A gnd! gnd! nmos w=1.4u l=0.35u

m2 z A vcc! vcc! pmos w=(1.4u*alpha) l=0.35u

.ends

3-13 (71)

Xinv1 ~~a~~ ^b ~~c~~ inv M=fan

5-4 (150)

Vin a gnd! ov PWL 0 ONs 1Ns 3 2ONs 3

7-35 (281)

.measure TRAN tphl_inv TRIG v(Xinv1,a)

VAL=1.5 RISE=1 TARG v(Xinv5.z)

VAL=1.5 FALL=1


not in

.OPTION MEASFORM=3



this manual

↑ ^{SV} ~~C~~ format

Analytical Derivation

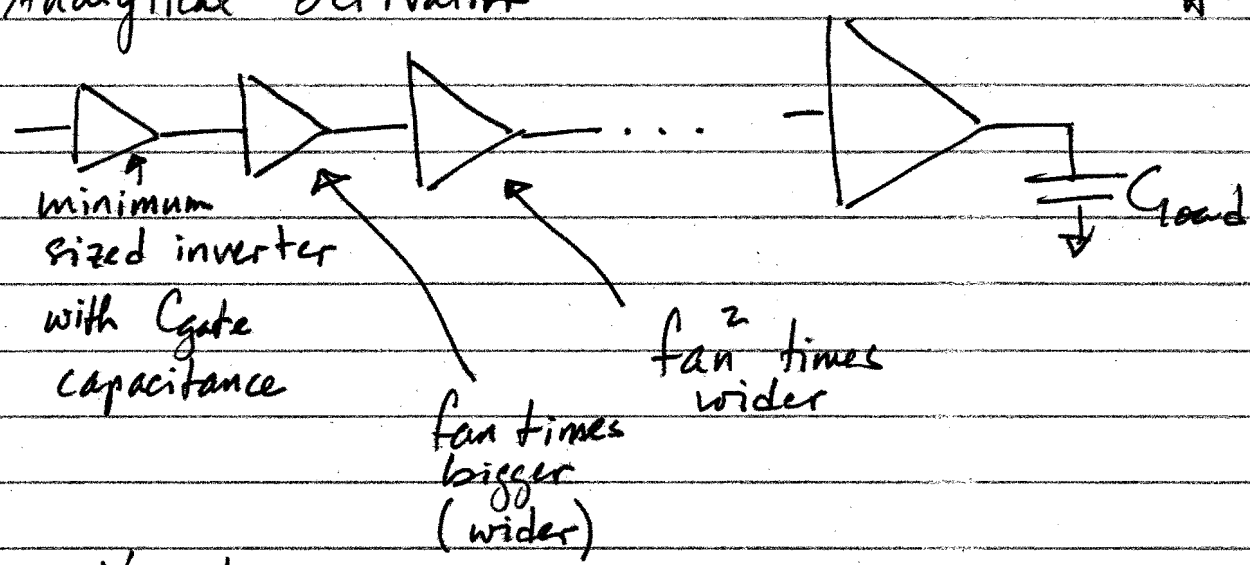

N stages

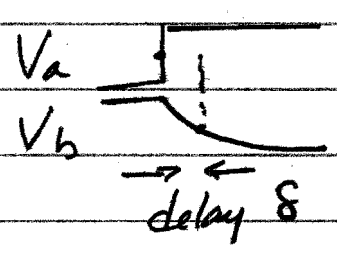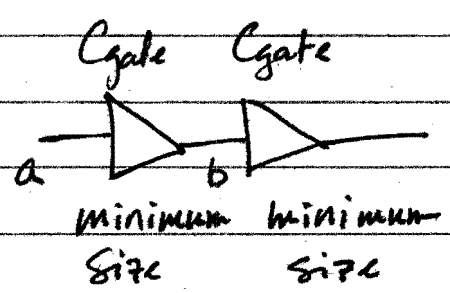

If second gate is fan times wider
 \rightarrow Delay = fan δ

$\frac{C_{load}}{C_{gate}} = fan^N$ for equal delays at each stage

* Ignoring Parasitics

dra
H-4

$$\text{total delay} \equiv D = N (\text{fan} \cdot \delta)$$

$$\text{but fan} = \left(\frac{C_{\text{load}}}{C_{\text{gate}}} \right)^{1/N} \quad R \equiv \frac{C_{\text{load}}}{C_{\text{gate}}}$$

$$D = N R^{1/N} \delta$$

for optimum delay $\frac{\partial D}{\partial N} = 0$

$$\frac{\partial}{\partial N} (N R^{1/N} \delta) = R^{1/N} \delta + N \frac{\partial}{\partial N} R^{1/N}$$

$$\begin{aligned} \frac{\partial}{\partial N} R^{1/N} &= \frac{\partial}{\partial N} e^{\ln R^{1/N}} = \frac{\partial}{\partial N} e^{\frac{1}{N} \ln R} \\ &= e^{\frac{1}{N} \ln R} \ln R \left(-\frac{1}{N^2} \right) = -R^{1/N} \frac{\ln R}{N^2} \end{aligned}$$

So

$$\frac{\partial D}{\partial N} = 0 = R^{1/N} \delta - N \delta R^{1/N} \frac{\ln R}{N^2} = R^{1/N} \delta \left(1 - \frac{\ln R}{N} \right)$$


$$\therefore \frac{\ln R}{N} = 1 \quad \ln R = N \quad R = e^N$$

$$\boxed{R^{1/N} = e = \text{fan} \quad \& N = \ln R}$$

But for practical circuits

drx
H-5

① we cannot ignore parasitics

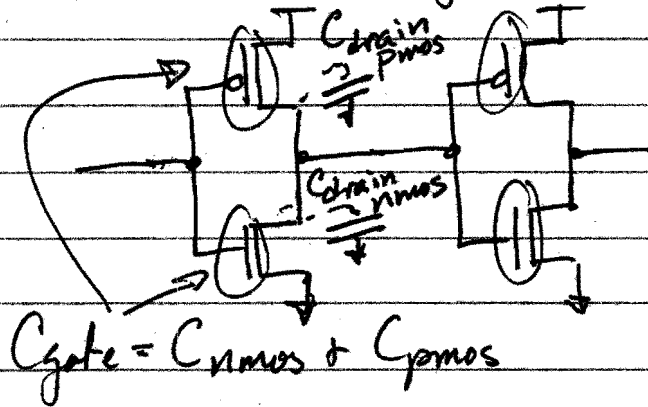

② using standard cells fan must be an integer

③ of course N , the number of stages, must be an integer

So, we need to write a python script to run hspice multiple times for slightly different input files searching for an optimum N & fan for a given CMOS technology & C_{load} .